

# Challenges & Solutions

As a beginner, developing this smart ultrasonic humidifier PCB was a significant learning experience. This section outlines the main technical challenges I encountered during the design and how I addressed or planned to address them.

---

## 1. Component Placement and Routing

### Challenge:

As this was my first attempt at designing a PCB, organizing components in a compact and logical way was difficult. I struggled with minimizing wire overlaps and ensuring correct pin-to-pin connectivity.

### Solution:

I referred to standard PCB layout practices and examples online, using KiCad's design rule checks to identify short circuits or disconnected traces. I grouped related components (e.g., oscillator circuit, power supply section) to maintain clarity and functionality.

---

## 2. EMI and Noise Handling

### Challenge:

Ultrasonic humidifiers operate using high-frequency oscillation which can introduce electromagnetic interference (EMI) into the circuit, especially around the microcontroller and communication module.

### Solution:

To reduce EMI:

- I used a decoupling capacitor (100nF) close to the ATmega328P's power supply pins.
  - I ensured short traces for power lines and critical components like the oscillator.
  - For future versions, I plan to add ground planes and shielding around sensitive components.
-

### 3. Moisture Exposure

**Challenge:**

Since the device operates in a humid environment, there is a risk of condensation or moisture affecting the PCB, causing shorts or corrosion.

**Solution:**

While my current version lacks full environmental sealing, I plan to:

- Apply a conformal coating to the PCB to protect traces and components.
  - Use an enclosure with IP-rated seals to shield the board from moisture.
  - Mount the PCB away from direct mist output from the humidifier.
- 

### 4. Power Supply Stability

**Challenge:**

Voltage fluctuations or power surges could damage the microcontroller or other sensitive components.

**Solution:**

I used the LM7805 voltage regulator for stable 5V output and added capacitors for filtering noise. In future iterations, I will include a diode for reverse polarity protection and an electrolytic capacitor for better power buffering.

---

### 5. Relay Driving Logic

**Challenge:**

Interfacing a 5V logic microcontroller with a relay safely was new to me. I was unsure about transistor selection and resistor sizing.

**Solution:**

I studied basic relay driving circuits using NPN transistors or MOSFETs. I selected appropriate base/gate resistors and ensured the use of a flyback diode (to be added in the final version) to protect against back-EMF from the relay coil.

---

## 6. Bluetooth Communication Reliability

### Challenge:

Ensuring reliable Bluetooth communication with HC-05 required stable UART signal levels and careful power regulation.

### Solution:

I matched the TX/RX pins correctly and plan to add level-shifting resistors in future versions to protect the module. I also ensured the HC-05 shared a common ground with the ATmega328P for stable operation.

---

## Conclusion

As a beginner, I faced many technical challenges, but with self-learning and experimentation, I was able to create a fully functional prototype. This project has greatly improved my confidence in hardware design and embedded systems.